

Experiment # 12

Circuit Analysis using MATLAB


Objectives:

Objectives of this lab is to analyze given circuit using MATLAB


Apparatus:

- Computer with PSPICE and MATLAB software installed on it

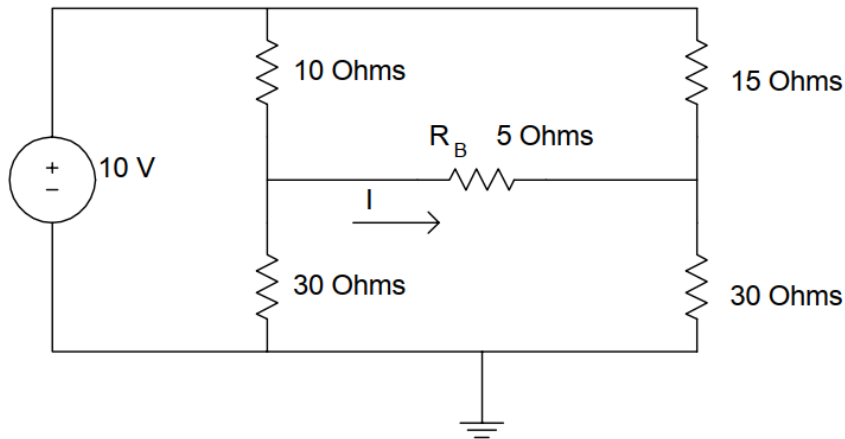Use the mesh analysis to find the current flowing through the resistor RB:



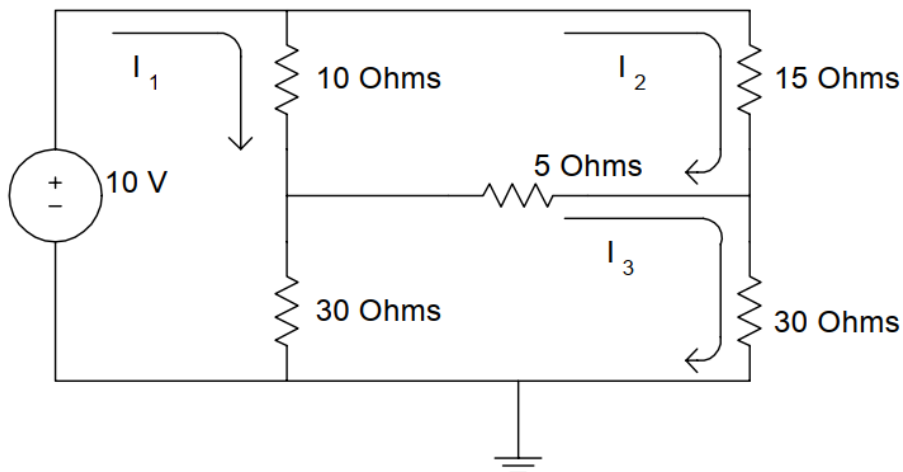Using loop analysis and designating the loop currents as I_1, I_2, I_3 , we obtain the following figure.



Note that $I = I_3 - I_2$

The loop equations are

Loop 1,

$$10(I_1 - I_2) + 30(I_1 - I_3) - 10 = 0$$

$$40I_1 - 10I_2 - 30I_3 = 10 \quad (4.22)$$

Loop 2,

$$10(I_2 - I_1) + 15I_2 + 5(I_2 - I_3) = 0$$

$$-10I_1 + 30I_2 - 5I_3 = 0 \quad (4.23)$$

Loop 3,

$$30(I_3 - I_1) + 5(I_3 - I_2) + 30I_3 = 0$$

$$-30I_1 - 5I_2 + 65I_3 = 0 \quad (4.24)$$

In matrix form, Equations (4.22) and (4.23) become

$$\begin{bmatrix} 40 & -10 & -30 \\ -10 & 30 & -5 \\ -30 & -5 & 65 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix} \quad (4.25)$$

MatLab Code:

```
lab13.m  X  +
1      % this program determines the current
2      % flowing in a resistor RB
3      % it computes the loop currents given the impedance
4      % matrix Z and voltage vector V
5      % Z is the impedance matrix
6      % V is the voltage matrix
7      % initialize the matrix Z and vector V
8 -    clc
9 -    clear all
10 -    Z = [40 -10 -30;
11         -10 30 -5;
12         -30 -5 65];
13 -    V = [10 0 0]';
14      % solve for the loop currents
15 -    I = inv(Z)*V;
16 -    fprintf('the current through I1 is %.3f Amps \n',I(1))
17 -    fprintf('the current through I2 is %.3f Amps \n',I(2))
18 -    fprintf('the current through I3 is %.3f Amps \n',I(3))
19      % current through RB is calculated
20 -    IRB = I(3) - I(2);
21 -    fprintf('the current through R is %.3f Amps \n',IRB)
```

Output:

```
Command Window
the current through I1 is 0.475 Amps
the current through I2 is 0.198 Amps
the current through I3 is 0.235 Amps
the current through R is 0.037 Amps
fx >> |
```

PSPICE Verification:

