

## Experiment # 6

### Verification of Kirchhoff's Voltage Law (KVL) using Breadboard

#### Objective:

To verify Kirchhoff's Voltage Law (KVL) on Breadboard and know relationship between varying resistors and applied voltage.

#### Apparatus:

1. DMM
2. Resistors
3. DC power supply

#### Procedure:

- 1) Design the following circuit on breadboard

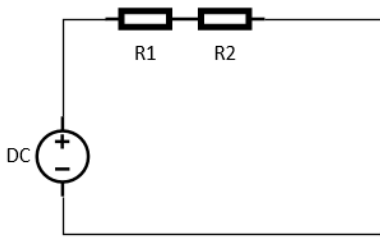


Figure 1 Circuit diagram

- 2) Using DMM find resistance of the resistors and note down in the table.
- 3) Find voltage of DC source and voltage drop on each resistor and note down in the table.
- 4) Add the voltage drops and compare with the source voltage by finding the percentage error.

#### Observation:

S.no	Vs (actual) (V)	R1 (Measured) ( $\Omega$ )	R2 (Measured) ( $\Omega$ )	V1 (Measured) (V)	V2 (Measured) (V)	V1+V2 (V)	Error	Percentage Error (%)
1.	5							
2.	10							

3.	15							
4.	20							
5.	30							